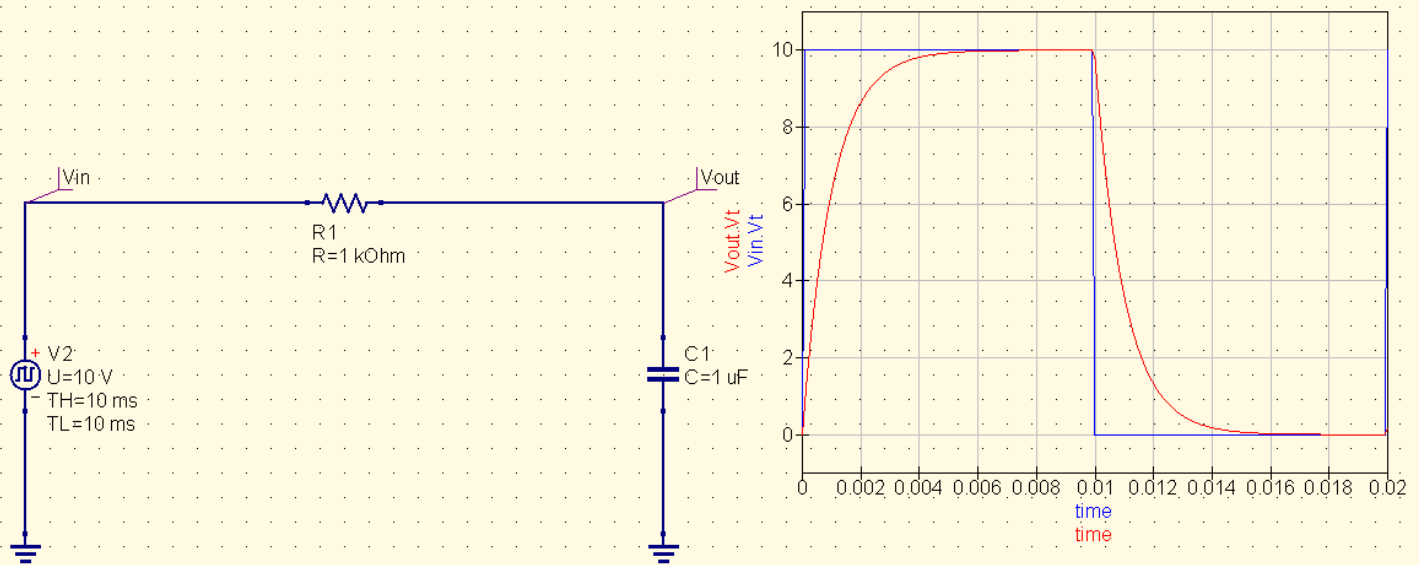



Question-1



transient
simulation



TR1
Type=lin
Start=0
Stop=20 ms

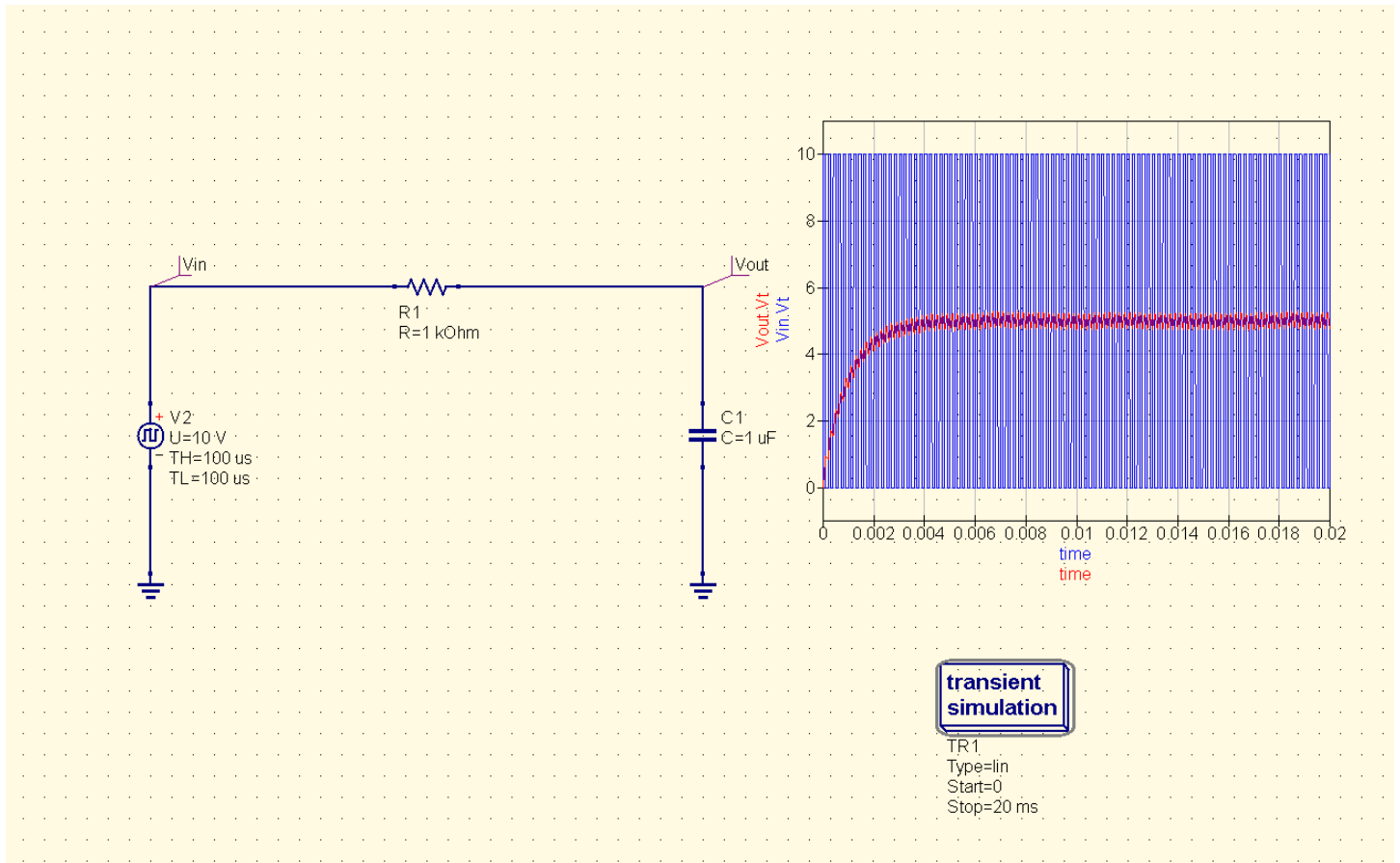Function of the circuit: This circuit acts as a voltage follower as $V_{in} = V_{out}$ for pulse frequency greater than or equal to 10 times the Time Constant (1ms).



Function of the circuit: This circuit acts as an integrator for pulse frequency lesser than the Time Constant (1ms).

Proof :

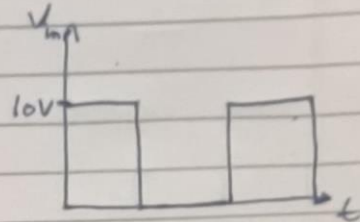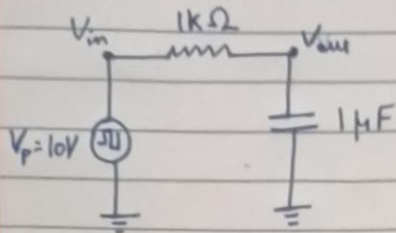

a) $\therefore \tau \ll T$, where $\tau = 1\text{ms}$

For +ve half cycle:-

$$\therefore V_{out} = 10(1 - e^{-t/\tau})$$

$$V_{out} \approx 10V$$

For -ve half cycle:-

$$V_{out} = 10e^{-t/\tau}$$

$$V_{out} \approx 0V$$

b) For $T \ll \tau$

1st half cycle:-

$$V_c = 10(1 - e^{-t/2RC})$$

$$V_c = [10(1 - e^{-t/2RC})] e^{-t/2RC} \quad (1^{st} \text{ cycle})$$

$$V_c = 1^{st} \text{ half cycle} + 1^{st} \text{ cycle}$$

$$= [10(1 - e^{-t/2RC})] e^{-t/2RC} + 10(1 - e^{-t/2RC}) \quad (\text{For } 1.5 \text{ cycle})$$


$$\text{let } e^{-t/2RC} = x$$

$$V_c = 10(1 - x + x^2 - x^3 \dots) \quad (\text{For } \infty \text{ cycles})$$

$$V_c = \frac{10(1)}{1+x} = \frac{10}{1+e^{-t/2RC}}$$

$$\therefore V_c = \frac{10}{1+1} = 5V \quad (t \ll 2RC)$$

Question-2

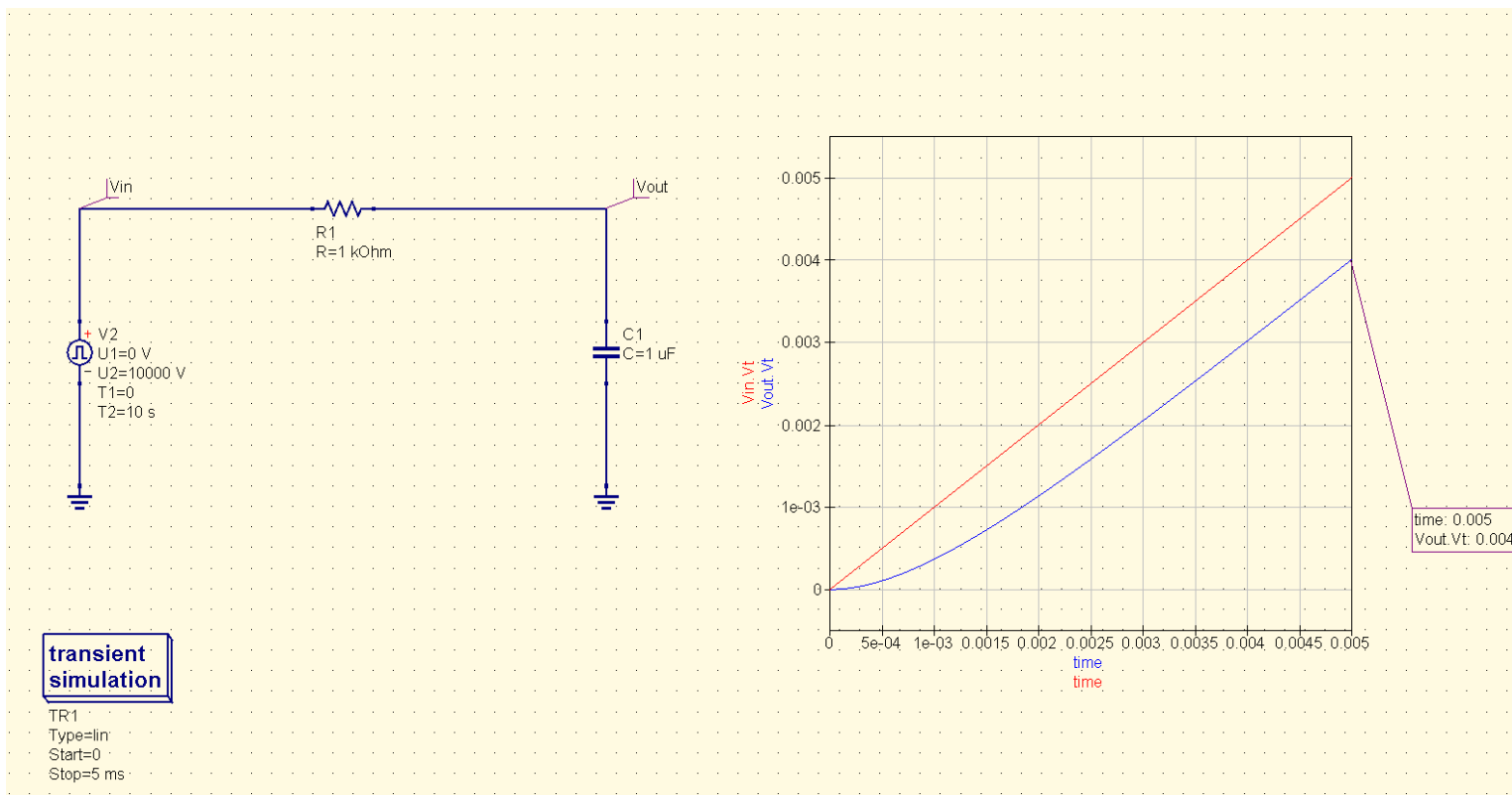

What happens in the circuit:

The capacitor delays (offsets) the input ramp voltage by 1mV.

Expected Output at V_{out} node:

$V_{out}(t) = V_{in}(t) - V_{in}(T)$, where $T = \text{Time Constant} = 1\text{ms}$

At $t = 5\text{ms}$, $t \gg T$:

$$\underline{V_{out}(5\text{ms})} = V_{in}(5\text{ms}) - 1\text{mV} = 5\text{mV} - 1\text{mV} = \underline{4\text{mV}}$$

Simulation Output at V_{out} : $\underline{V_{out}(5\text{ms}) = 4\text{mV}}$